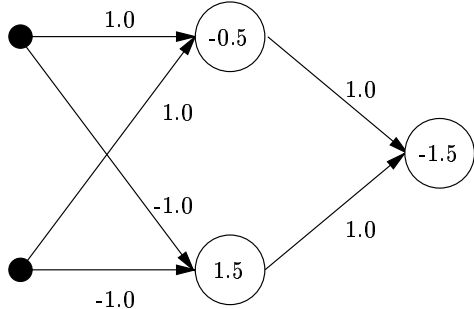


(a)



(b)

**Figure 22.6** A two-layer perceptron solves XOR: (a) the solution as a digital circuit, and (b) weight and bias values for a perceptron that emulates the XOR circuit